

Solving Problems: Ohm's Law

OHM'S LAW

Current (amps, A) $I = \frac{V}{R}$ ***Voltage*** (volts, V)
Resistance (ohms, Ω)