

Short Circuit

A large amount of current passes through the short circuit branch. Almost no current goes through the bulb.

