

Solving Problems: Voltage in Series Circuits

Each resistance drops the voltage

